



**Digital Filters IIR** (& Their Corresponding Analog Filters)

ELEC 3004: Systems: Signals & Controls

Dr. Surya Singh

Lecture 10

elec3004@itee.uq.edu.au

http://robotics.itee.uq.edu.au/~elec3004/

April 4, 2017

(CC)) BY-NC-SA

# Lecture Schedule:

Week	Date	Lecture Title			
1	28-Feb	Introduction			
1	2-Mar	Systems Overview			
2	7-Mar	Systems as Maps & Signals as Vectors			
2	9-Mar	Systems: Linear Differential Systems			
3	14-Mar	Sampling Theory & Data Acquisition			
3	16-Mar	Aliasing & Antialiasing			
4	21-Mar	Discrete Time Analysis & Z-Transform			
-4		Second Order LTID (& Convolution Review)			
5	28-Mar	Frequency Response			
3	30-Mar	Filter Analysis			
6	4-Apr	Digital Filters (IIR) & Filter Analysis			
U	6-Apr	Digital Windows			
_		Digital Filter (FIR)			
7	13-Apr				
	18-Apr				
	20-Apr	Holiday			
	25-Apr				
8	27-Apr	Active Filters & Estimation			
9	2-May	Introduction to Feedback Control			
	4-May	Servoregulation/PID			
10		Introduction to (Digital) Control			
10		Digitial Control			
11		Digital Control Design			
- 1		Stability			
12		Digital Control Systems: Shaping the Dynamic Response			
.2		Applications in Industry			
13		System Identification & Information Theory			
,	1-Jun	Summary and Course Review			

ELEC 3004: Systems

# Follow Along Reading:



B. P. Lathi Signal processing and linear systems 1998 TK5102.9.L38 1998

#### Today

- Chapter 10
  - (Discrete-Time System Analysis Using the z-Transform)
  - § 10.3 Properties of DTFT
  - § 10.5 Discrete-Time Linear System analysis by DTFT
  - § 10.7 Generalization of DTFT to the Z-Transform
- Chapter 12
  - (Frequency Response and Digital Filters)
- § 12.1 Frequency Response of Discrete-Time Systems
- § 12.3 Digital Filters
- § 12.4 Filter Design Criteria
- § 12.7 Nonrecursive Filters

Next Time

ELEC 3004: Systems

4 April 2017

# Announcements: Cyclone Debbie






- Lecture 10: Cancelled (Sorry!)
  - We will makeup some of the material today! ☺


Sources: [L] http://www.abc.net.au/news/2017-03-28/cyclone-debbie--space-stations-capture-incredible-images/8392232 [R] Mr. Fausto Benavides


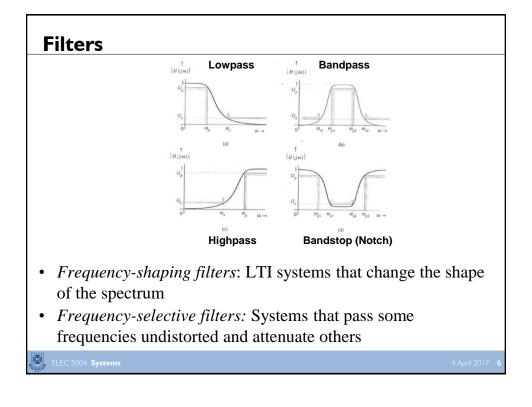
# Let's Start With: (analog) Filters! ELEC 3004: Systems 4 April 2017 5



# **Filters**

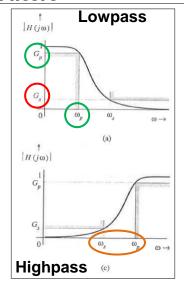

#### Specified Values:

• **Gp** = minimum passband gain Typically:

$$G_p = \frac{1}{\sqrt{2}} = -3dB$$

- Gs = maximum stopband gain
  - Low, not zero (sorry!)
  - For realizable filters, the gain cannot be zero over a finite band (Paley-Wiener condition)
- Transition Band:
   transition from the passband to the stopband → ωp≠ ωs



4 April 2017 **7** 

# Filter Design & z-Transform

Filter Type	Mapping	Design Parameters
Low-pass	$z^{-1} \to \frac{z^{-1} - \alpha}{1 - \alpha z^{-1}}$	$\alpha = \frac{\sin[(\omega_c - \omega_c')/2]}{\sin[(\omega_c + \omega_c')/2]}$
High-pass	$z^{-1} \rightarrow -\frac{z^{-1} + \alpha}{1 + \alpha z^{-1}}$	$\omega'_c$ = desired cutoff frequency $\alpha = -\frac{\cos[(\omega_c + \omega'_c)/2]}{\cos[(\omega_c - \omega'_c)/2]}$ $\omega'_c$ = desired cutoff frequency
Bandpass	$z^{-1} \to -\frac{z^{-2} - [2\alpha\beta/(\beta+1)]z^{-1} + [(\beta-1)/(\beta+1)]}{[(\beta-1)/(\beta+1)]z^{-2} - [2\alpha\beta/(\beta+1)]z^{-1} + 1}$	$\alpha = \frac{\cos[(\omega_{c2} + \omega_{c1})/2]}{\cos[(\omega_{c2} - \omega_{c1})/2]}$ $\beta = \cot[(\omega_{c2} - \omega_{c1})/2] \tan(\omega_{c}/2)$
Bandstop	$z^{-1} \rightarrow \frac{z^{-2} - [2\alpha/(\beta+1)]z^{-1} + [(1-\beta)/(1+\beta)]}{[(1-\beta)/(1+\beta)]z^{-2} - [2\alpha/(\beta+1)]z^{-1} + 1}$	$\begin{aligned} \omega_{c1} &= \text{desired lower cutoff frequency} \\ \omega_{c2} &= \text{desired upper cutoff frequency} \\ \alpha &= \frac{\cos[(\omega_{c1} + \omega_{c2})/2]}{\cos[(\omega_{c1} - \omega_{c2})/2]} \\ \beta &= \tan[(\omega_{c2} - \omega_{c1})/2] \tan(\omega_{c}/2) \end{aligned}$
		$\omega_{c1}$ = desired lower cutoff frequency $\omega_{c2}$ = desired upper cutoff frequency



1 April 2017

#### **Butterworth Filters**

- Butterworth: Smooth in the pass-band
- The amplitude response  $|H(j\omega)|$  of an n<sup>th</sup> order Butterworth low pass filter is given by:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}}$$


• The normalized case ( $\omega_c=1$ )

$$|\mathcal{H}(j\omega)| = \frac{1}{\sqrt{1+\omega^{2n}}}$$
  $\mathcal{H}(j\omega)\mathcal{H}(-j\omega) = |\mathcal{H}(j\omega)|^2 = \frac{1}{1+\omega^{2n}}$ 

Recall that:  $|H(j\omega)|^2 = H(j\omega) H(-j\omega)$ 




4 April 2017

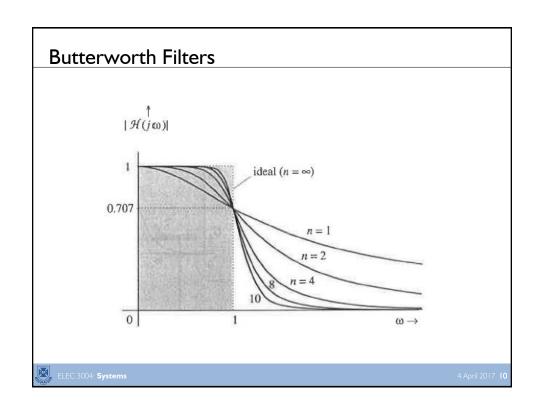

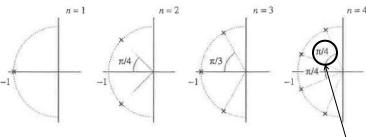
# Butterworth Filters of Increasing Order: Seeing this Using a Pole-Zero Diagram

• Increasing the order, increases the number of poles:




- $\rightarrow$  Odd orders (n=1,3,5...):
- Have a pole on the Real Axis
- $\rightarrow$  Even orders (n=2,4,6...):
- Have a pole on the off axis

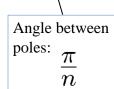


ELEC 3004: Systems

4 April 2017 |

# Butterworth Filters: Pole-Zero Diagram

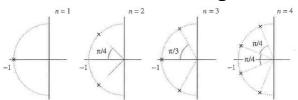

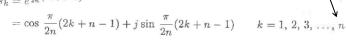
- Since H(s) is stable and causal, its poles must lie in the LHP
- Poles of -H(s) are those in the RHP
- Poles lie on the unit circle (for a normalized filter)
- →  $H(s) = \frac{1}{(s s_1)(s s_2)...(s s_n)}$ Where:  $s_k = e^{\frac{j\pi}{2n}(2k + n - 1)}$



n is the order of the filter


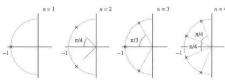
# Butterworth Filters: 4th Order Filter Example



• Plugging in for n=4, k=1,...4:

$$\mathcal{H}(s) = \frac{1}{(s+0.3827 - j0.9239)(s+0.3827 + j0.9239)(s+0.9239 - j0.3827)(s+0.9239 + j0.3827)}$$

$$= \frac{1}{(s^2+0.7654s+1)(s^2+1.8478s+1)}$$

$$= \frac{1}{s^4+2.6131s^3+3.4142s^2+2.6131s+1}$$

• We can generalize → Butterworth Table

n	$a_1$	$a_1$ $a_2$		$a_1$ $a_2$ $a_3$		a4	$a_5$
2	1.41421356						
3	2.00000000	2.00000000					
4	2.61312593	3.41421356	2.61312593				
5	3.23606798	5.23606798	5.23606798	3.23606798			
6	3.86370331	7.46410162	9.14162017	7.46410162	3.86370331		

This is for 3dB bandwidth at  $\omega_c$ =1

4 April 2017 **13** 

# Butterworth Filters: Scaling Back (from Normalized)

- Start with Normalized equation & Table
- Replace  $\omega$  with  $\frac{\omega}{\omega_c}$  in the filter equation
- For example: for  $f_c$ =100Hz  $\rightarrow \omega_c$ =200 $\pi$  rad/sec

From the Butterworth table: for n=2,  $a_1 = \sqrt{2}$  Thus:

$$H(s) = \frac{1}{\left(\frac{s}{200\pi}\right)^2 + \sqrt{2}\left(\frac{s}{200\pi}\right) + 1}$$
$$= \frac{1}{s^2 + 200\pi\sqrt{2} + 40,000\pi^2}$$

ELEC 3004: Systems

#### Butterworth: Determination of Filter Order

- Define  $G_x$  as the gain of a lowpass Butterworth filter at  $\omega = \omega_x$
- Then:

$$\hat{G}_x = 20 \log_{10} |H(j\omega_x)| = -10 \log \left[ 1 + \left( \frac{\omega_x}{\omega_c} \right)^{2n} \right]$$

And thus:

$$\hat{G}_p = -10 \log \left[ 1 + \left( \frac{\omega_p}{\omega_c} \right)^{2n} \right]$$

$$\hat{G}_s = -10 \log \left[ 1 + \left( \frac{\omega_s}{\omega_c} \right)^{2n} \right]$$

Or alternatively:

$$\omega_c = \frac{\omega_p}{\left[10^{-\tilde{G}_p/10^{\circ}} - 1\right]^{1/2n}} \quad \& \quad \omega_c = \frac{\omega_s}{\left[10^{-\tilde{G}_s/10} - 1\right]^{1/2n}}$$

Solving for n gives:


$$n = \frac{\log \left[ \left( 10^{-\hat{G}_s/10} - 1 \right) / \left( 10^{-\hat{G}_p/10} - 1 \right) \right]}{2 \log(\omega_s/\omega_p)}$$


PS. See Lathi 4.10 (p. 453) for an example in MATLAB

ELEC 3004: Systems

4 April 2017 15

# Chebyshev Filters

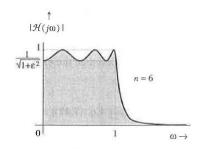

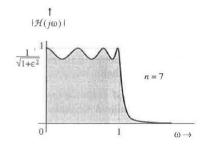

• equal-ripple:

Because all the ripples in the passband are of equal height

• If we reduce the ripple, the passband behaviour improves, but it does so at the cost of stopband behaviour

ELEC 3004: Systems

4.4--:12017.14

#### Chebyshev Filters

- Chebyshev Filters: Provide tighter transition bands (sharper cutoff) than the sameorder Butterworth filter, but this is achieved at the expense of inferior passband behavior (rippling)
- $\rightarrow$  For the lowpass (LP) case: at higher frequencies (in the stopband), the Chebyshev filter gain is smaller than the comparable Butterworth filter gain by about  $\underline{6(n-1)}$  dB
- The amplitude response of a normalized Chebyshev lowpass filter is:

$$|\mathcal{H}(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_n^2(\omega)}}$$

Where  $Cn(\omega)$ , the nth-order Chebyshev polynomial, is given by:

$$C_n(\omega) = \cos(n\cos^{-1}\omega)$$

$$C_n(\omega) = \cosh(n\cosh^{-1}\omega)$$
and where  $C_n$  is given by:
$$\begin{array}{c}
n & C_n(\omega) \\
0 & 1 \\
1 & \omega \\
2 & 2\omega^2 - 1 \\
3 & 4\omega^3 - 3\omega \\
4 & 8\omega^4 - 8\omega^2 + 1 \\
5 & 16\omega^5 - 20\omega^3 + 5\omega \\
6 & 32\omega^6 - 48\omega^4 + 18\omega^2 - 1
\end{array}$$



4 April 2017 17

# Normalized Chebyshev Properties

- It's normalized: The passband is  $0<\omega<1$
- Amplitude response: has ripples in the passband and is smooth (monotonic) in the stopband
- Number of ripples: there is a total of n maxima and minima over the passband  $0<\omega<1$

• 
$$C_n^2(0) = \begin{cases} 0, & n : odd \\ 1, & n : even \end{cases}$$
  $|H(0)| = \begin{cases} \frac{1}{\sqrt{1+\epsilon^2}}, & n : even \end{cases}$ 

- $\epsilon$ : ripple height  $\rightarrow r = \sqrt{1 + \epsilon^2}$
- The Amplitude at  $\omega = 1$ :  $\frac{1}{r} = \frac{1}{\sqrt{1+c^2}}$
- For Chebyshev filters, the ripple r dB takes the place of  $G_p$



#### **Determination of Filter Order**

- The gain is given by:  $\hat{G} = -10 \log \left[1 + \epsilon^2 C_n^2(\omega)\right]$ Thus, the gain at  $\omega_s$  is:  $\epsilon^2 C_n^2(\omega_s) = 10^{-\hat{G}_s/10} - 1$
- Solving:

$$n = \frac{1}{\cosh^{-1}(\omega_s)} \cosh^{-1} \left[ \frac{10^{-\hat{G}_s/10} - 1}{10^{\hat{r}/10} - 1} \right]^{1/2}$$

• General Case:

$$n = \frac{1}{\cosh^{-1}(\omega_s/\omega_p)} \cosh^{-1} \left[ \frac{10^{-\hat{G}_s/10} - 1}{10^{\hat{\tau}/10} - 1} \right]^{1/2}$$

ELEC 3004: Systems

4 April 2017 19

# Chebyshev Pole Zero Diagram

Whereas <u>Butterworth</u> poles lie on a <u>semi-circle</u>,
 The poles of an n<sup>th</sup>-order normalized <u>Chebyshev</u> filter lie on a <u>semiellipse</u> of the major and minor semiaxes:

$$a = \sinh\left(\frac{1}{n} \sinh^{-1}\left(\frac{1}{\epsilon}\right)\right) \quad \& \quad b = \cosh\left(\frac{1}{n} \sinh^{-1}\left(\frac{1}{\epsilon}\right)\right)$$


And the poles are at the locations:

$$H\left(s\right) = \frac{1}{\left(s - s_1\right)\left(s - s_2\right)\dots\left(s - s_n\right)}$$

$$s_k = -\sin\left[\frac{(2k - 1)\pi}{2n}\right]\sinh x + j\cos\left[\frac{(2k - 1)\pi}{2n}\right]\cosh x, \ k = 1,\dots, n$$

ELEC 3004: Systems
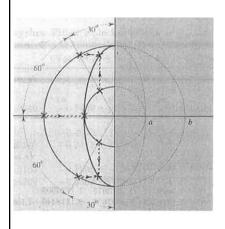
# Ex: Chebyshev Pole Zero Diagram for n=3



#### Procedure:

- 1. Draw two semicircles of radii **a** and **b** (from the previous slide).
- 2. Draw radial lines along the corresponding Butterworth angles  $(\pi/n)$  and locate the n<sup>th</sup>-order Butterworth poles (shown by crosses) on the two circles.
- 3. The location of the k<sup>th</sup> Chebyshev pole is the intersection of the horizontal projection and the vertical projection from the corresponding k<sup>th</sup> Butterworth poles on the outer and the inner circle, respectively.

ELEC 3004: Systems

4 April 2017 **2** 

# Chebyshev Values / Table

$$\mathcal{H}(s) = \frac{K_n}{C'_n(s)} = \frac{K_n}{s^n + a_{n-1}s^{n-1} + \dots + a_1s + a_0}$$

$$K_n = \begin{cases} a_0 & n \text{ odd} \\ \frac{a_0}{\sqrt{1 + \epsilon^2}} = \frac{a_0}{10^{\hat{r}/20}} & n \text{ even} \end{cases}$$

n	$a_0$	$a_1$	$a_2$	<i>a</i> <sub>3</sub>
1	1.9652267			
2	1.1025103	1.0977343		
3	0.4913067	1.2384092	0.9883412	
4	0.2756276	0.7426194	1.4539248	0.9528114

1 db ripple  $(\hat{r} = 1)$ 



4 A---12017 **22** 

#### Other Filter Types:

# **Chebyshev Type II** = Inverse Chebyshev Filters

- Chebyshev filters passband has ripples and the stopband is smooth.
- Instead: this has passband have smooth response and ripples in the stopband.
- → Exhibits maximally flat passband response and equi-ripple stopband
- → Cheby2 in MATLAB

$$|\mathcal{H}(\omega)|^2=1-|\mathcal{H}_C(1/\omega)|^2=\frac{\epsilon^2C_n^2(1/\omega)}{1+\epsilon^2C_n^2(1/\omega)}$$
 Where: H<sub>c</sub> is the Chebyshev filter system from before

- Passband behavior, especially for small  $\omega$ , is **better** than Chebyshev
- **Smallest transition band** of the 3 filters (Butter, Cheby, Cheby2)
- Less time-delay (or phase loss) than that of the **Chebyshev**
- Both needs the **same order** *n* to meet a set of specifications.
- **\$\$\$** (or number of elements): Cheby < Inverse Chebyshev < Butterworth (of the same performance [not order])



# Other Filter Types:

## **Elliptic Filters (or Cauer) Filters**

- Allow **ripple** in **both** the passband and the stopband,
  - we can achieve **tighter** transition band

$$|\mathcal{H}(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 R_n^2(\omega)}}$$


 $\mathbf{R}_{\mathbf{n}}$  is the n<sup>th</sup>-order Chebyshev rational function determined from a given ripple spec.  $\epsilon$  controls the ripple

- Most efficient (n)
  - the **largest ratio** of the passband gain to stopband gain
  - or for a given ratio of passband to stopband gain, it requires the smallest transition band
- → in MATLAB: ellipord followed by ellip

# In Summary

Filter Type	Passband Ripple	Stopband Ripple	Transition Band	MATLAB Design Command
Butterworth	No	No	Loose	butter
Chebyshev	Yes	No	Tight	cheby
Chebyshev Type II (Inverse Chebyshev)	No	Yes	Tight	cheby2
Eliptic	Yes	Yes	Tightest	ellip



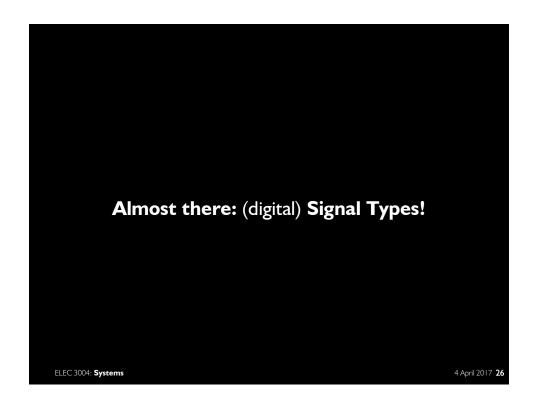

# Impulse Response of Both Types


$$y[n] = \frac{1}{2}u[n-1] + \frac{1}{2}u[n]$$

$$h[n]$$

$$\frac{1}{2} \qquad \frac{1}{2}$$

$$n$$

'Finite impulse response" (FIR)

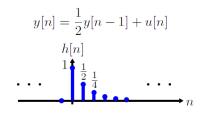

"Infinite impulse response" (IIR)

ELEC 3004: Systems

4 April 2017 **27** 

# → Digital Filters Types

#### FIR

From H(z):

→ Filter becomes a "multiply, accumulate, and delay" system:


$$y(t) = \sum_{\tau=0}^{n-1} h_{\tau} u(t-\tau)$$

$$y[n] = b_0 x[n] + b_1 x[n-1] + \dots + b_N x[n-N]$$

$$x[n] \xrightarrow{x[n]} b_s \xrightarrow{y_{b_s}} b_s \xrightarrow{y_{b_s}} b_s \xrightarrow{y_{b_s}} y_{[n]}$$

#### <u>IIR</u>

• <u>Impulse response</u> function that is non-zero over an infinite length of time.

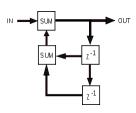

ELEC 3004: Systems

#### **FIR Properties**

- Require no feedback.
- Are inherently stable.
- They can easily be designed to be <u>linear phase</u> by making the coefficient sequence symmetric
- Flexibility in shaping their magnitude response
- Very Fast Implementation (based around FFTs)
- The main disadvantage of FIR filters is that considerably more computation power in a general purpose processor is required compared to an IIR filter with similar sharpness or <u>selectivity</u>, especially when low frequency (relative to the sample rate) cutoffs are needed.



4 April 2017 **29** 

#### FIR as a class of LTI Filters

• Transfer function of the filter is

$$H(z) = \frac{Y(z)}{X(z)} = \frac{\sum_{k=0}^{M} b_k z^{-k}}{1 + \sum_{k=1}^{N} a_k z^{-k}}$$

- Finite Impulse Response (FIR) Filters: (N = 0, no feedback)
- $\rightarrow$  From H(z):

$$H(\omega) = h_0 + h_1 e^{-i\omega} + \dots + h_{n-1} e^{-i(n-1)\omega}$$
$$= \sum_{t=0}^{n-1} h_t \cos t\omega - i \sum_{t=0}^{n-1} h_t \sin t\omega$$


- $\because$  H( $\omega$ ) is periodic and conjugate
- $\therefore \underline{\text{Consider } \omega \in [0, \pi]}$


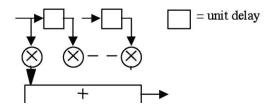
#### FIR Filters

- Let us consider an FIR filter of length M
- Order *N*=*M*-1 (watch out!)
- Order → number of delays

$$y(n) = \sum_{k=0}^{M-1} b_k x(n-k) = \sum_{k=0}^{M-1} h(k) x(n-k)$$





4 April 2017 3

# FIR Impulse Response

Obtain the impulse response immediately with  $x(n) = \delta(n)$ :


$$h(n) = y(n) = \sum_{k=0}^{M-1} b_k \delta(n-k) = b_n$$

- The impulse response is of finite length M (good!)
- FIR filters have only zeros (no poles) (as they must, N=0 !!)
   Hence known also as all-zero filters
- FIR filters also known as feedforward or non-recursive, or transversal filters

ELEC 3004: Systems

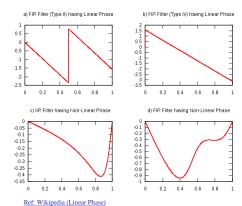
#### FIR & Linear Phase

- The <u>phase response</u> of the filter is a <u>linear</u> function of frequency
- Linear phase has constant group delay, all frequency components have equal delay times. ∴ No distortion due to different time delays of different frequencies




• FIR Filters with:

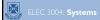
$$\sum_{n=-\infty}^{\infty} h[n] \cdot \sin(\omega \cdot (n-\alpha) + \beta) = 0$$



4 April 2017 3

# FIR & Linear Phase → Four Types

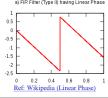

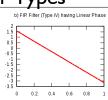


Impulse response	# coefs	$H\left(\omega ight)$	Type
$h\left(n\right) = h\left(M - 1 - n\right)$	Odd	$e^{-j\omega(M-1)/2} \left( h\left(\frac{M-1}{2}\right) + 2\sum_{k=1}^{(M-3)/2} h\left(\frac{M-1}{2} - k\right) \cos(\omega k) \right)$	1
$h\left(n\right) = h\left(M - 1 - n\right)$	Even	$e^{-j\omega(M-1)/2} 2 \sum_{k=1}^{(M-3)/2} h\left(\frac{M}{2} - k\right) \cos\left(\omega\left(k - \frac{1}{2}\right)\right)$	2
h(n) = -h(M - 1 - n)	Odd	$e^{-j[\omega(M-1)/2-\pi/2]} \left(2\sum_{k=1}^{(M-1)/2} h\left(\frac{M-1}{2}-k\right)\sin(\omega k)\right)$	3
h(n) = -h(M - 1 - n)	Even	$e^{-j[\omega(M-1)/2-\pi/2]} 2 \sum_{k=1}^{(M-1)/2} h\left(\frac{M}{2}-k\right) \sin\left(\omega\left(k-\frac{1}{2}\right)\right)$	4

- Type 1: most versatile
- Type 2: frequency response is always 0 at ω=π (not suitable as a high-pass)
- Type 3 and 4: introduce a  $\pi/2$  phase shift, 0 at  $\omega=0$  (not suitable as a high-pass)





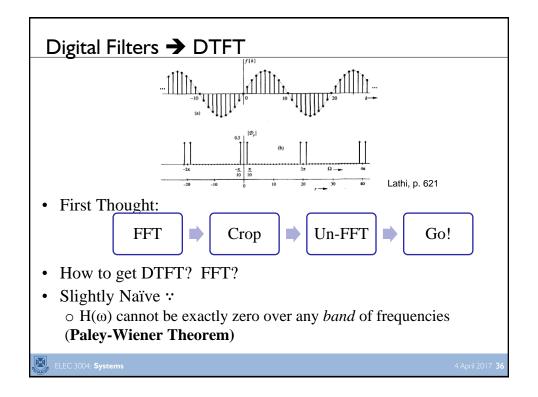



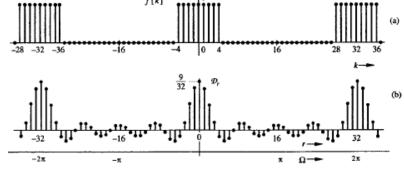


Fig. 10.2 Periodic sampled gate pulse and its Fourier spectrum. Lathi, p. 623

- The frequency response is limited to  $2\pi$

DTFT is a convolution responses in time domain... 
$$\underbrace{\mathcal{F}\{x*h\}}_{Y(\omega)} = \underbrace{\mathcal{F}\{x\}}_{X(\omega)} \cdot \underbrace{\mathcal{F}\{h\}}_{H(\omega)}$$
$$y[n] = x[n]*h[n] = \mathcal{F}^{-1}\{X(\omega) \cdot H(\omega)\},$$

ELEC 3004: Systems

# DTFT > z-Transform

The above results motivate the definitions of the z transform, the discrete-time Fourier transform (DTFT), and the discrete Fourier series (DFS) to be presented in this chapter and the next. In particular, if the basis functions for the input can be enumerated as

$$\phi_k[n] = z_k^n,$$

that is, if x(t) can be expressed in the form of Eq. (6.1.1) as

$$x[n] = \sum_{k} a_k z_k^n, (6.1.10)$$

then the corresponding output is simply, from Eqs. (6.1.2) and (6.1.8),

$$y[n] = \sum_{k} a_{k} H(z_{k}) z_{k}^{n}. \tag{6.1.11}$$

The discrete Fourier series for periodic signals is of this form, with  $z_k = e^{j2\pi k/N}$ . If, on the other hand, the required basis functions cannot be enumerated, we must utilize the continuum of functions  $\phi[n] = z^n$  to represent x[n] and y[n] in the form of integrals. When z is restricted to have unit magnitude (that is,  $z = e^{j\Omega}$ ), the resulting representation is called the discrete-time Fourier transform, while if z is an arbitrary complex variable, the full z-transform representation results.

#### The Discrete-Time Fourier Transform

• Synthesis:

The function  $X(e^{j\Omega})$  defined by

$$X(e^{j\Omega}) = \sum_{n=-\infty}^{\infty} x[n]e^{-j\Omega n}$$
 (7.1.1)

(if it converges) is called the discrete-time Fourier transform (DTFT) of the signal x[n]. In particular, if the region of convergence for the z transform

$$X(z) = \sum_{n=-\infty}^{\infty} x[n]z^{-n}$$

includes the unit circle, then the DTFT equals X(z) evaluated on the unit circle, that is,

$$X(e^{j\Omega}) = X(z)|_{z=e^{j\Omega}}. (7.1.2)$$

ELEC 3004: Systems

4 April 2017 39

# The Discrete-Time Fourier Transform

• Analysis/Inverse:

$$x[n] = \frac{1}{2\pi} \int_{2\pi} X(e^{j\Omega}) e^{j\Omega n} d\Omega.$$

- x[n] is the (limiting) sum of sinusoidal components of the form  $\left[\frac{1}{2\pi}X(e^{j\Omega})d\Omega\right]e^{j\Omega n}$
- Together: Forms the DTFT Pair

ELEC 3004: Systems

#### The Discrete-Time Fourier Transform

• Ex:

$$x[n] = a^n u[n]$$

has the z transform

$$X(z) = \frac{1}{1 - az^{-1}}, \quad |z| > |a|,$$

and thus  $X(e^{i\Omega})$  exists for |a|<1 because the ROC then contains the unit circle. Specifically,

$$X(e^{j\Omega}) = \frac{1}{1 - ae^{-j\Omega}}, \qquad |a| < 1.$$
 (7.1.8)

The corresponding magnitude spectrum  $|X(e^{j\Omega})|$  and phase spectrum  $\angle X(e^{j\Omega})$  are shown in Fig. 6.8. Clearly, from the defining sum in Eq. (7.1.1), the DTFT of x[n] does not converge for |a| > 1, and we defer until later the case of |a| = 1.

On the other hand, the anticausal exponential

$$w[n] = -a^n u[-n-1]$$

has the z transform

$$W(z) = \frac{1}{1 - az^{-1}}, \qquad |z| < |a|,$$

and thus  $W(e^{j\Omega})$  exists for |a| > 1, but not for |a| < 1. That is,

$$W(e^{j\Omega}) = \frac{1}{1 - ae^{-j\Omega}}, \quad |a| > 1.$$
 (7.1.9)

Again the case of |a| = 1 is deferred until later.



#### The Discrete-Time Fourier Transform

• Observe:

"Kinship Of Difference Equations To Differential Equations"

$$\frac{dy}{dt} + cy(t) = x(t) \tag{3.15a}$$

Consider uniform samples of x(t) at intervals of T seconds. As usual, we use the notation x[n] to denote x(nT), the nth sample of x(t). Similarly, y[n] denotes y[nT], the nth sample of y(t). From the basic definition of a derivative, we can express Eq. (3.15a) at t = nT as  $\lim_{T \to 0} \frac{y[n] - y[n-1]}{T} + cy[n] = x[n]$ 

$$\lim_{T \to 0} \frac{y[n] - y[n-1]}{T} + cy[n] = x[n]$$

Clearing the fractions and rearranging the terms yields (assuming nonzero, but very small  $\mathcal{T}$ )

$$y[n] + \alpha y[n-1] = \beta x[n] \tag{3.15b}$$

where 
$$\alpha = \frac{-1}{1+cT}$$
 and  $\beta = \frac{T}{1+cT}$ 

We can also express Eq. (3.15b) in advance operator form as

$$y[n+1] + \alpha y[n] = \beta x[n+1]$$
 (3.15c)

#### The Discrete-Time Fourier Transform

• Ex(2): The DTFT of the real sinusoid

$$x[n] = \sin \Omega_0 n = \frac{1}{2j} (e^{j\Omega_0 n} - e^{-j\Omega_0 n})$$

is simply

$$X(e^{j\Omega}) = 2\pi \left(\frac{1}{2j}\right) [\delta(\Omega - \Omega_0) - \delta(\Omega + \Omega_0)]$$

$$=-j\pi[\delta(\Omega-\Omega_0)-\delta(\Omega+\Omega_0)]$$

for  $|\Omega|$ ,  $|\Omega_0| \le \pi$ , while that of the cosine signal

$$y[n] = \cos \Omega_0 n = \frac{1}{2} (e^{j\Omega_0 n} + e^{-j\Omega_0 n})$$

is likewise

$$Y(e^{j\Omega}) = 2\pi(\frac{1}{2})[\delta(\Omega - \Omega_0) + \delta(\Omega + \Omega_0)]$$
  
=  $\pi[\delta(\Omega - \Omega_0) + \delta(\Omega + \Omega_0)].$ 


In addition, the DTFT pair for the dc signal x[n] = 1 is simply

$$1 \leftrightarrow 2\pi \, \delta(\Omega), \qquad |\Omega| \leq \pi,$$


as opposed to the dual relationship

$$\delta[n] \leftrightarrow 1$$
, all  $\Omega$ .

ELEC 3004: Systems

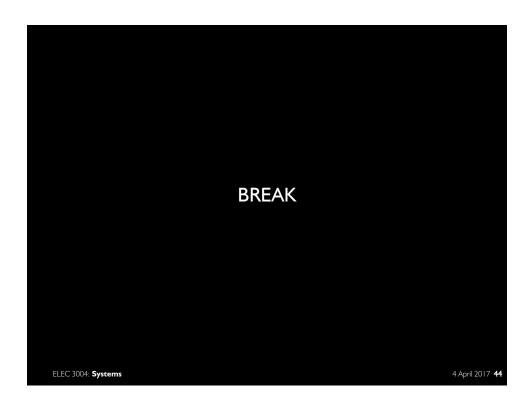




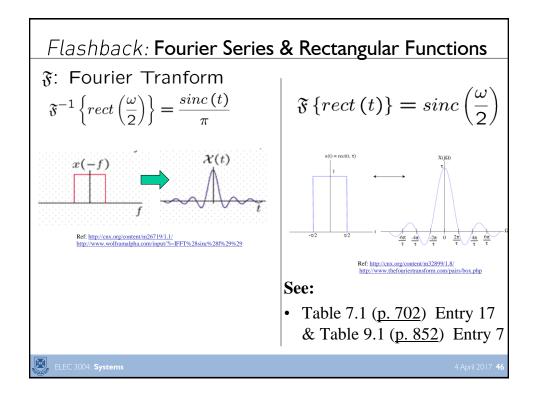
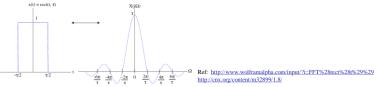
# Flashback: Fourier Series & Rectangular Functions [2]

- The sinc function might look familiar
  - This is the frequency content of a square wave (box)



- This also applies to **signal reconstruction!**
- → Whittaker–Shannon interpolation formula
  - This says that the "better way" to go from Discrete to Continuous
     (i.e. D to A) is not ZOH, but rather via the sinc!

$$x(t) = \sum_{n=-\infty}^{\infty} x[n] \cdot \operatorname{sinc}\left(\frac{t-nT}{T}\right)$$




4 April 2017 **4**7

# Filter Design

- Previously we have analysed
  - difference equations (y[n])
  - transfer functions (H(z))
- To obtain time/frequency domain response
  - Impulse (h[n]) or frequency (H(w)) response
- Now we have a specification
  - frequency response (filters)
  - time response (control)
- Goal to design a filter that meets specification
  - i.e., determine transfer function
  - and therefore difference equation (implementation)

ELEC 3004: Systems

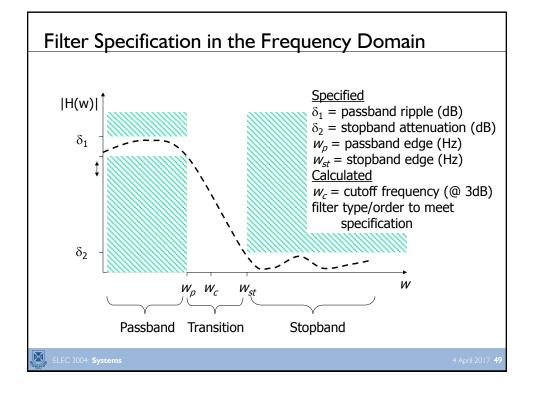

# Transfer Function → Difference Equation

• Example, consider

ELEC 3004: Systems

$$H(z) = \frac{z^2 - 0.2z - 0.08}{z^2 + 0.5}$$
 Make H(z) causal × by  $\frac{z^{-2}}{z^{-2}}$ 


Normalise to negative powers of z (causal)
 re-arrange and take inverse z transform


$$H(z) = \frac{1 - 0.2z^{-1} - 0.08z^{-2}}{1 + 0.5z^{-2}} = \frac{Y(z)}{X(z)}$$


$$Y(z)(1 + 0.5z^{-2}) = X(z)(1 - 0.2z^{-1} - 0.08z^{-2})$$

$$y[n] + 0.5y[n - 2] = x[n] - 0.2x[n - 1] - 0.08x[n - 2]$$
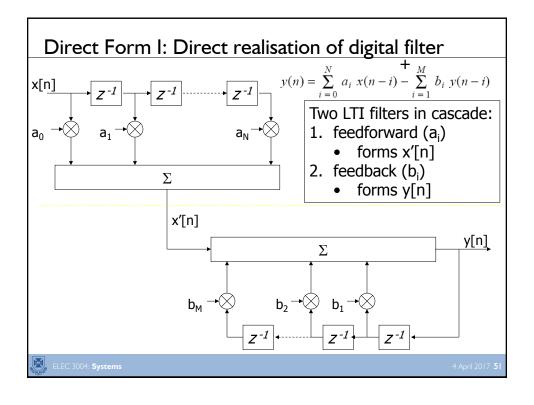
$$y[n] = x[n] - 0.2x[n - 1] - 0.08x[n - 2] - 0.5y[n - 2]$$



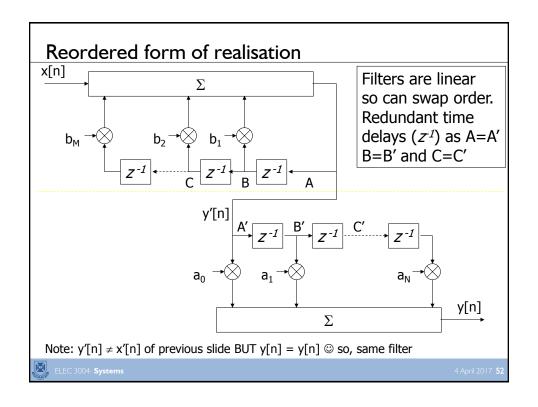

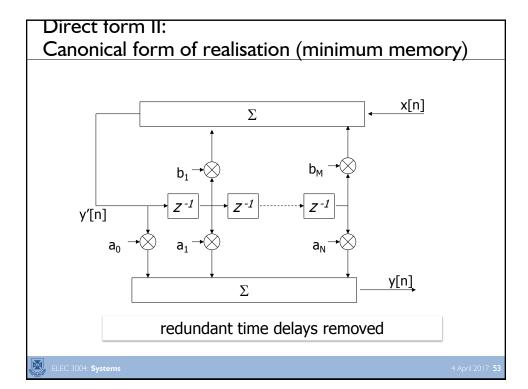

# Derivation of Canonical Form

$$H(z) = \frac{Y(z)}{X(z)} = \frac{\sum_{i=0}^{N} a_i z^{-i}}{(1 - \sum_{i=1}^{M} b_i z^{-i})}$$

General form of transfer function

$$Y(z) = H(z) X(z)$$

Re-arranging in terms of output

$$Y(z) = \sum_{i=0}^{N} a_i z^{-i} Y'(z)$$

$$Y(z) = \sum_{i=0}^{N} a_i z^{-i} \ Y'(z)$$
 where  $Y'(z) = \frac{X(z)}{(1 - \sum_{i=1}^{M} b_i z^{-i})}$ 

Which as a difference equation is

 $y(n) = \sum_{i=0}^{N} a_i \ y'(n-i)$  where  $y'(n) = x(n) + \sum_{i=1}^{M} b_i \ y'(n-i)$ , Direct II

 $y(n) = \sum_{i=0}^{N} a_i \ x(n-i) + \sum_{i=1}^{M} b_i \ y(n-i)$ Direct I


Canonical terms

A' B' C'


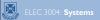
#### Canonical Realisation


- Direct Form I
  - Conceptually simplest realisation
  - Often less susceptible to noise
- Canonical/Direct Form II
  - Minimimum memory (storage)
- Filter design
  - Determine value of filter coefficients (all ai & bi)
  - Poles controlled by bi coefficients
    - if any  $bi \neq 0$  then filter IIR (recursive)
    - if all bi = 0 then filter FIR (non-recursive)
  - Zeros controlled by ai coefficients



4 April 2017 **55** 
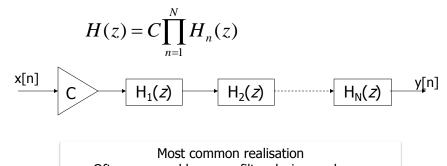
#### Cascade Form

- Transfer function factorised to
  - Product of second order terms Hn(z)
  - C is a constant (gain)




Often assumed by many filter design packages many 2<sup>nd</sup> order sections have integer coefficients



#### **Parallel Form**

- Transfer function expressed as
  - partial fraction expansion of second order terms

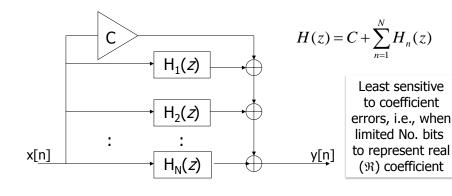


ELEC 3004: Systems

4 400012017
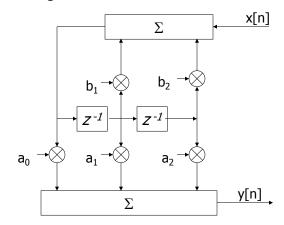
# Bi-quadratic Digital Filter

- Canonic form of Second order system
- 2nd order, system 'building block'




Difference equation:

$$y[n] = a_0x[n] + a_1x[n-1] + a_2x[n-2] + b_1y[n-1] + b_2y[n-2]$$

ELEC 3004: Systems
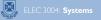
#### IIR Filter Design Methods

- Normally based on analogue prototypes
  - Butterworth, Chebyshev, Elliptic etc
- Then transform  $H(s) \rightarrow H(z)$
- Three popular methods:
- Impulse invariant
  - produces H(z) whose impulse response is a sampled version of h(t) (also step invariant)
- Matched z transform
  - poles/zeros H(s) directly mapped to poles/zeros H(z)
- Bilinear z transform
  - left hand s plane mapped to unit circle in z plane



4 April 2017 59

# Impulse Invariant

- Simplest approach, proceeds as follows,
- Select prototype analogue filter
- Determine H(s) for desired wc and ws
- Inverse Laplace,
  - i.e., calculate impulse response, h(t)
- Sample impulse response  $h(t)|t=n\Delta td$ 
  - $h[n] = \Delta td h(n\Delta td)$
- Take z transform of  $h[n] \Rightarrow H(z)$ 
  - poles, p1 map to  $exp(p1\Delta td)$  (maintains stability)
  - zeros have no simple mapping



# Impulse Invariant

- Useful approach when
  - Impulse (or step) invariance is required, or
    - e.g., control applications
  - Designing Lowpass or Bandpass filters
- · Has problems when
  - H(w) does not  $\rightarrow 0$  as w  $\rightarrow \infty$
  - i.e., if H(w) is not bandlimited, aliasing occurs
  - e.g., highpass or bandstop filters



4 April 2017 6

#### Matched z - transform

- Maps poles/zeros in s plane directly
  - − to poles/zeros in z − plane
- No great virtues/problems
- · Fairly old method
  - not commonly used
  - so we won't consider it further

ELEC 3004: Systems


#### Bilinear z - transform

- Maps complete imaginary s –plane  $(\pm \infty)$ 
  - to unit circle in z -plane
- i.e., maps analogue frequency wa to
  - discrete frequency wd
- uses continuous transform,

$$w_a = \frac{2}{\Delta t} \tan \left( \frac{w_d \Delta t}{2} \right)$$

This compresses (warps)  $w_a$  to have finite extent  $\pm w_g/2$  i.e., this removes possibility of any aliasing  $\odot$ 

ELEC 3004: Systems

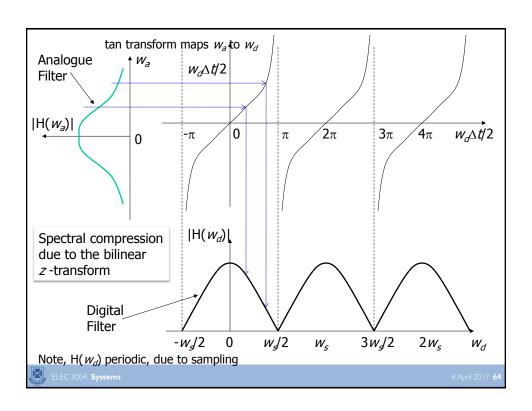

# Bilinear Transform

$$\omega_a = \frac{2}{\Delta t} \tan(\frac{\omega_d \Delta t}{2})$$

The bilinear transform

$$s = \frac{2}{\Delta t} \frac{j \sin(\frac{\omega_d \Delta t}{2})}{\cos(\frac{\omega_d \Delta t}{2})}$$

Transforming to s-domain Remember:  $s = j\omega_a$  and  $tan\theta = sin\theta/cos\theta$  Where  $\theta = \omega_d \Delta t/2$ 

$$s = \frac{2}{\Delta t} \frac{\frac{1}{2}(\exp(\frac{j\omega_d \Delta t}{2}) - \exp(\frac{-j\omega_d \Delta t}{2}))}{\frac{1}{2}(\exp(\frac{j\omega_d \Delta t}{2}) + \exp(\frac{-j\omega_d \Delta t}{2}))}$$

Using Euler's relation This becomes... (note: j terms cancel)

$$s = \frac{2}{\Delta t} \frac{(1 - \exp(-j\omega_d \Delta t))}{(1 + \exp(-j\omega_d \Delta t))}$$

Multiply by  $\exp(-j\theta)/\exp(-j\theta)$ 

$$s = \frac{2(1 - z^{-1})}{\Delta t (1 + z^{-1})}$$

As  $z = \exp(s_d \Delta t) = \exp(j\omega_d \Delta t)$ 



4 April 2017 65

#### Bilinear Transform

• Convert  $H(s) \Rightarrow H(z)$  by substituting,

$$s = \frac{2(1 - z^{-1})}{\Delta t (1 + z^{-1})}$$


• However, this transformation compressive frequency response, which means

Note: this comes directly from **tan** transform

- digital cut off frequency will be lower than the analogue prototype
- Therefore, analogue filter must be "pre-warped" prior to transforming H(s) ⇒ H(z)

ELEC 3004: Systems

# Bilinear Pre-warping

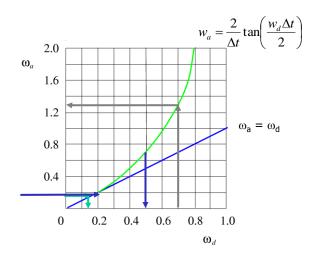

ELEC 3004: Systems

# Bilinear Transform: Example

- Design digital Butterworth lowpass filter
  - order, n = 2, cut off frequency wd = 628 rad/s
  - sampling frequency ws = 5024 rad/s (800Hz)
- pre-warp to find wa that gives desired wd

desired wd
$$w_a = \left(\frac{2}{1/800}\right) \tan\left(\frac{628}{2 \times 800}\right) = 663 \text{ rad/s} \quad \text{Note: } w_d < w_a \text{ due to compression}$$

• Butterworth prototype (unity

cut off) is,

$$H(s) = \frac{1}{s^2 + \sqrt{2}s + 1}$$

ELEC 3004: Systems

# Bilinear Transform: Example

- De-normalised analogue prototype (s' = s/ $\omega_c$ )
  - $\omega_c = 663 \, rad/s$  (required  $\omega_a$  to give desired)

$$H(s_d) = \frac{1}{\left(\frac{s}{663}\right)^2 + \frac{\sqrt{2}s}{663} + 1}$$

- Convert  $H(s) \Rightarrow H(z)$  by substituting

$$H(z) = \frac{1}{\left(\frac{2 \times 800(1-z^{-1})}{663(1+z^{-1})}\right)^2 + \sqrt{2}\left(\frac{2 \times 800(1-z^{-1})}{663(1+z^{-1})}\right) + 1}$$

$$H(z) = \frac{0.098z^2 + 0.195z + 0.098}{z^2 - 0.942z + 0.333}$$

Note: H(z) has both poles and zeros H(s) was all-pole

ELEC 3004: Systems

Bilinear Transform: Example
$$H(z) = \frac{Y(z)}{X(z)} = \frac{0.098z^2 + 0.195z + 0.098}{z^2 - 0.942z + 0.333}$$


Multiply out and make causal:


$$Y(z)(z^{2}-0.942z+0.333) = X(z)(0.098z^{2}+0.195z+0.098)$$
$$Y(z)(1-0.942z^{-1}+0.333z^{-2}) = X(z)(0.098+0.195z^{-1}+0.098z^{-2})$$


Finally, apply inverse z-transform to yield the difference equation:


$$y[n] = 0.098x[n] + 0.195x[n-1] + 0.098x[n-2] + 0.942y[n-1] - 0.333y[n-2]$$


ELEC 3004: System

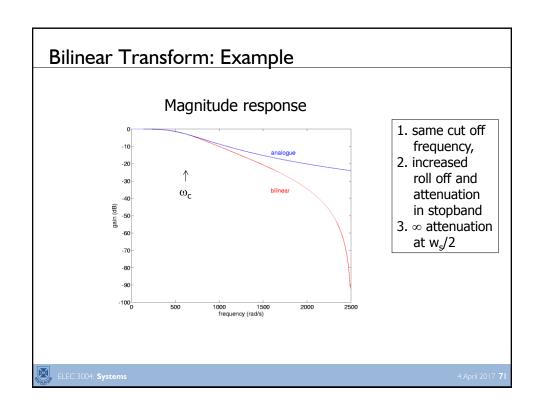

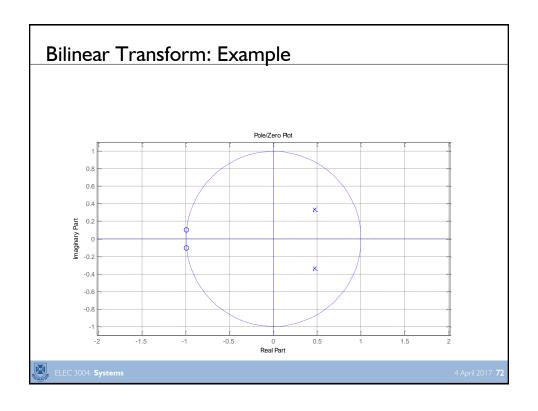

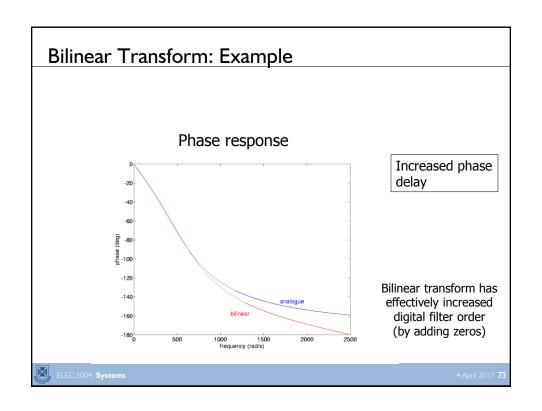

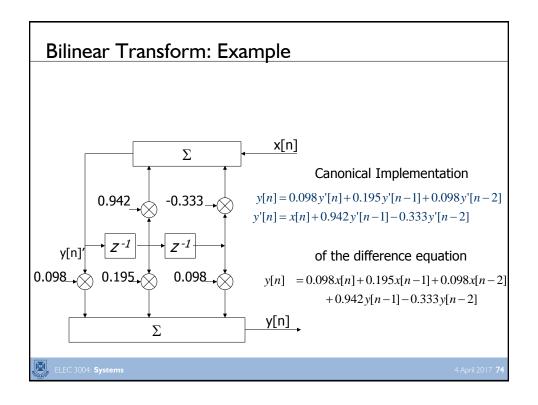

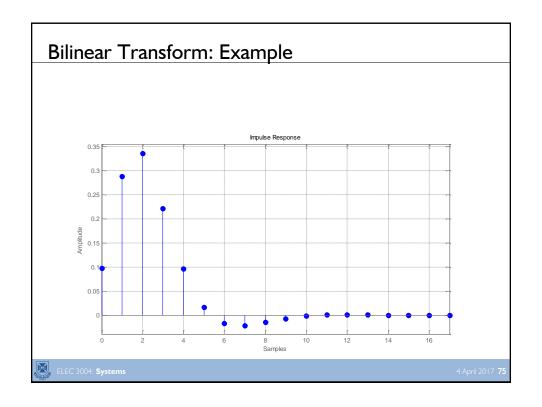


# Bilinear Design Summary

- Calculate pre-warping analogue cutoff frequency
- De-normalise filter transfer function using pre-warping cut-off
- Apply bilinear transform and simplify
- Use inverse z-transform to obtain difference equation

ELEC 3004: Systems
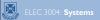
#### **Direct Synthesis**

- Not based on analogue prototype
  - But direct placement of poles/zeros
- Useful for
  - First order lowpass or highpass
    - · simple smoothers
  - Resonators and equalisers
    - single frequency amplification/removal
  - Comb and notch filters
    - Multiple frequency amplification/removal



4 April 2017 **77** 

# First Order Filter: Example

- General first order transfer function
  - Gain, G, zero at -b, pole at a (a, b both < 1)


Remember: 
$$H(w) = H(z)|_{z = \exp(jw\Delta t)}$$

$$H(z) = \frac{G(1 + bz^{-1})}{(1 - az^{-1})}$$

with a +ve & b -ve this is a lowpass filter

$$H(0) = \frac{G(1+b)}{(1-a)}$$
  $\exp(j\pi) = -1$ 
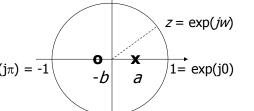
$$H(\pi) = \frac{G(1-b)}{(1+a)} \quad \omega_s/2$$





# First Order Filter: Example

- Possible design criteria
  - cut-off frequency, wc
    - $3dB = 20 \log(|H(wc)|)$
    - e.g., at wc =  $\pi/2$ ,  $(1+b)/(1+a) = \sqrt{2}$
  - stopband attenuation
    - assume wstop =  $\pi$  (Nyquist frequency)
    - e.g.,  $\delta 2 = H(\pi)/H(0) = 1/21$  i.e.,

$$\frac{H(\pi)}{H(0)} = \frac{(1-b)(1-a)}{(1+b)(1+a)} = \frac{1}{21}$$


two unknowns (*a,b*) two (simultaneous) design equations.



4 April 2017 **79** 
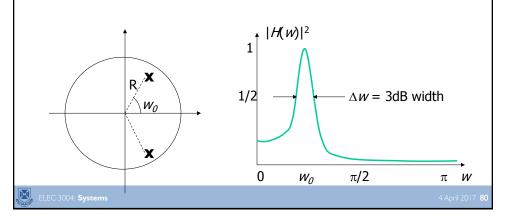
# Digital Resonator

- Second order 'resonator'
  - single narrow peak frequency response
  - i.e., peak at resonant frequency, w0



# Quality factor (Q-factor)

- Dimensionless parameter that compares
  - Time constant for oscillator decay/bandwidth ( $\Delta\omega$ ) to
  - Oscillation (resonant) period/frequency (ω0)
    - High Q = less energy dissipated per cycle

$$Q = \frac{\omega_0}{\Delta \omega} = \frac{f_0}{\Delta f}$$

• Alternative to damping factor ( $\zeta$ ) as

$$Q = \frac{1}{2\zeta} \qquad H(s) = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2} = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

• Note:  $Q < \frac{1}{2}$  overdamped (not an oscillator)

ELEC 3004: Systems

4 April 2017 8

# Digital Resonator Design

- To make a peak at w0 place pole
  - Inside unit circle (for stability)
  - At angle w0 distance R from origin
    - i.e., at location  $p = R \exp(jw0)$ 
      - R controls Δw
        - » Closer to unit circle  $\rightarrow$  sharper peak
    - plus complex conj pole at p\* = R exp(-jw0)

$$H(z) = \frac{1}{(1 - R \cdot \exp(jw_0)z^{-1})(1 - R \cdot \exp(-jw_0)z^{-1})}$$

$$= \frac{1}{1 - R(\exp(jw_0) + \exp(-jw_0))z^{-1} + R^2z^{-2}}$$

$$= \frac{G}{1 + a_1z^{-1} + a_2z^{-2}}$$


Where (via Euler's relation)

$$a_1 = -2R\cos(w_0)$$
 and  $a_2 = R^2$ 




# Discrete Filter Transformations


- By convention, design Lowpass filters
  - transform to HP, BP, BS, etc
- Simplest transformation
  - Lowpass H(z') → highpass H(z)
  - $HHP(z) = HLP(z)|z' \rightarrow -z|$ 
    - reflection about imaginary axis (ws/4)
    - changing signs of poles and zeros
- LP cutoff frequency, wCLP becomes
  - HP cut-in frequency, wCHP =  $\frac{1}{2}$  wCLP

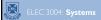
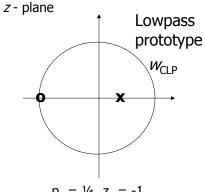
# Lowpass $\rightarrow$ highpass (z' = -z)



$$p_L = \frac{1}{4}, z_L = -1$$

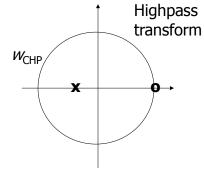

$$p_{H} = -\frac{1}{4}, z_{H} = 1$$

Poles/zeros reflected in imaginary axis:  $W_{CHP} = \frac{1}{2} - W_{CLP}$ Same gain @  $w_s/4$  (i.e.,  $\pi/4$ )  $|H(w_{HP})| = |H(\pi/2 - w_{LP})|$ 



#### Discrete Filter Transformations

- H(z)
  - Cut-off (3dB) frequency = wc (remains same)
- Lowpass  $H(z') \rightarrow highpass$  Lowpass  $H(z') \rightarrow Bandpass$ H(z)
  - Centre frequency = w0 & 3dB bandwidth = wc

$$z' = \frac{\cos(w_c \Delta t) - z}{1 - \cos(w_c \Delta t)z}$$

$$z' = \frac{\alpha z - z^2}{-\alpha z + 1} \qquad \alpha = \frac{\cos(w_0 \Delta t)}{\cos(w_c \Delta t)}$$

Note: these are not the only possible BP and BS transformations!



#### Discrete Filter Transformations


- Lowpass  $H(z') \rightarrow Bandstop H(z)$ 
  - Centre frequency = w0 3dB bandwidth = wc

$$z' = \frac{z^2 - (2\alpha/(k+1))z + (1-k)/(1+k)}{1 + (2\alpha/(k+1))z + ((1-k)/(1+k))z^2}$$

$$\alpha = \frac{\cos(w_0 \Delta t)}{\cos(w_c \Delta t)} \qquad k = \tan^2(w_c \Delta t)$$

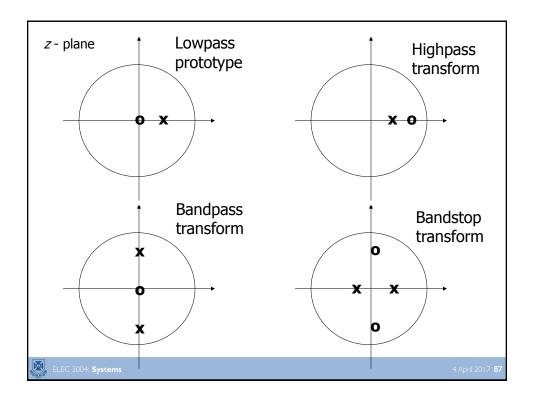Note: order doubles for bandpass/bandstop transformations





# Summary

- Digital Filter Structures
  - Direct form (simplest)
  - Canonical form (minimum memory)
- IIR filters
  - Feedback and/or feedforward sections
- FIR filters
  - Feedforward only
- Filter design
  - Bilinear transform (LP, HP, BP, BS filters)
  - Direct form (resonators and notch filters)
  - Filter transformations (LP  $\rightarrow$  HP, BP, or BS)
- Stability & Precision improved
  - Using cascade of 1st/2nd order sections

ELEC 3004: Systems

# Next Time...



• Digital Filters

- Review:
  - Chapter 10 of Lathi
- A signal has many signals © [Unless it's bandlimited. Then there is the one ω]

